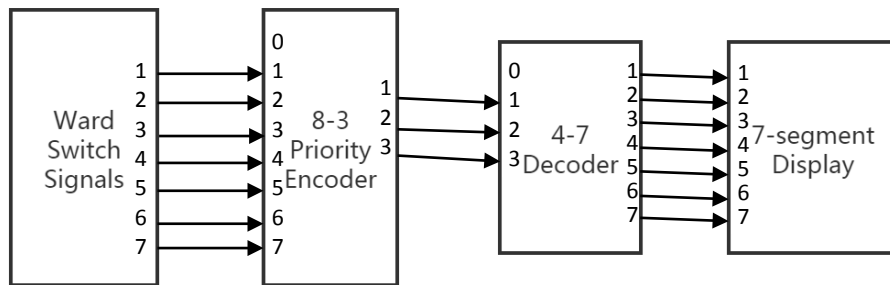


Assignment 2

Task 1

Block diagram



Task 2

VHDL code

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity encoder_8_3 is
5  port (encoder_in:  in  std_logic_vector(7 downto 0);
6       encoder_out:  out std_logic_vector(2 downto 0));
7  end encoder_8_3;
8
9  architecture design_encoder_8_3 of encoder_8_3 is
10 begin
11     encoder_out <= "000" when encoder_in(7) = '1' else
12                    "111" when encoder_in(6) = '1' else
13                    "110" when encoder_in(5) = '1' else
14                    "101" when encoder_in(4) = '1' else
15                    "100" when encoder_in(3) = '1' else
16                    "011" when encoder_in(2) = '1' else
17                    "010" when encoder_in(1) = '1' else
18                    "001" when encoder_in(0) = '1' else
19                    "000";
20
21 end design_encoder_8_3;
22
23 library ieee;
24 use ieee.std_logic_1164.all;
25
26 entity decoder_4_7 is
27 port (decoder_in:  in  std_logic_vector(3 downto 0);
28       decoder_out:  out std_logic_vector(6 downto 0));
29 end decoder_4_7;
30
31 architecture design_decoder_4_7 of decoder_4_7 is
32 begin
33     with decoder_in select
34         decoder_out <= "1111110" when "0000",
35                        "0110000" when "0001",
36                        "1101101" when "0010",
37                        "1111001" when "0011",
38                        "0110011" when "0100",
39                        "1011011" when "0101",
40                        "1011111" when "0110",
41                        "1110000" when "0111",
42                        "1111111" when "1000",
43                        "1111011" when "1001",
44                        "0000000" when others;
45
46 end design_decoder_4_7;
47
48 library ieee;
49 use ieee.std_logic_1164.all;
50
```


```

50
51 entity ward_switch_7 is
52 port( input: in std_logic_vector(7 downto 0);
53       output: out std_logic_vector(6 downto 0);
54       signal_3: out std_logic_vector(2 downto 0));
55 end ward_switch_7;
56
57 architecture design_ward of ward_switch_7 is
58
59 component encoder_8_3 is
60 port (encoder_in: in std_logic_vector(7 downto 0);
61       encoder_out: out std_logic_vector(2 downto 0));
62 end component;
63
64 component decoder_4_7 is
65 port (decoder_in: in std_logic_vector(3 downto 0);
66       decoder_out: out std_logic_vector(6 downto 0));
67 end component;
68
69 signal encoder_3 : std_logic_vector(2 downto 0);
70
71 begin
72 encoder: encoder_8_3 port map (input, encoder_3);
73 decoder: decoder_4_7 port map ('0' & encoder_3, output);
74
75 signal_3 <= encoder_3;
76
77 end design_ward;

```

Task 3


Test

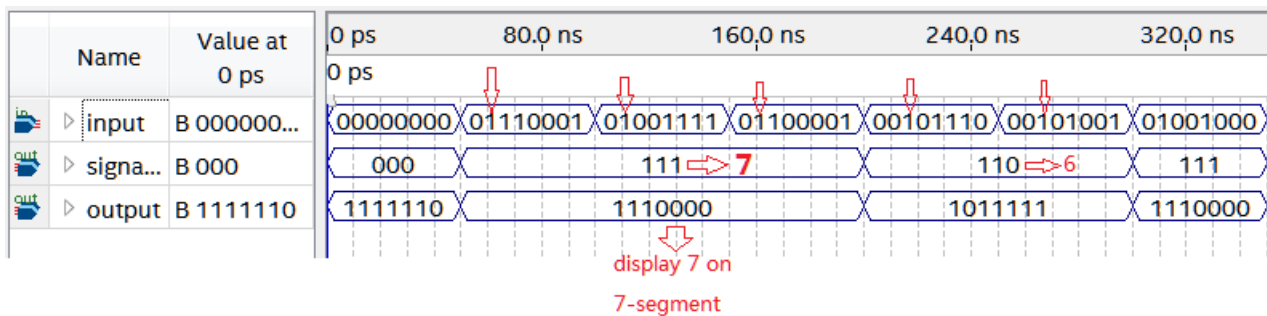

As shown, “input” is an 8-bit signal that shows which wards have alerted. The most left bit represents ward number 1.


“signal” is a 3-bit signal produced by 8-3 encoder. It shows the priority number of wards.

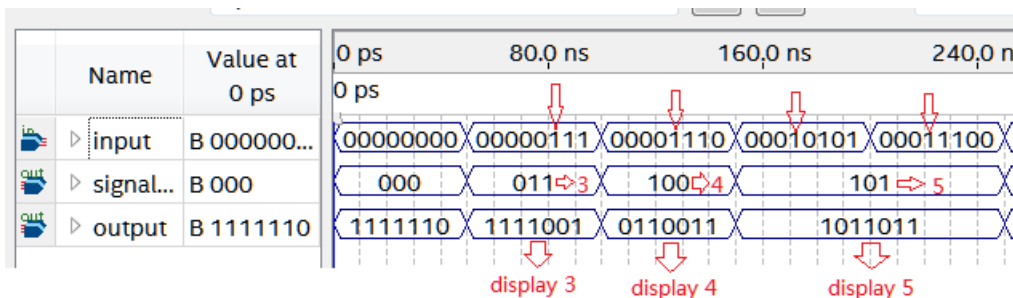“output” is a 7-bit signal which can be sent to 7-segment display to show the corresponding number.



More test result.

diagram

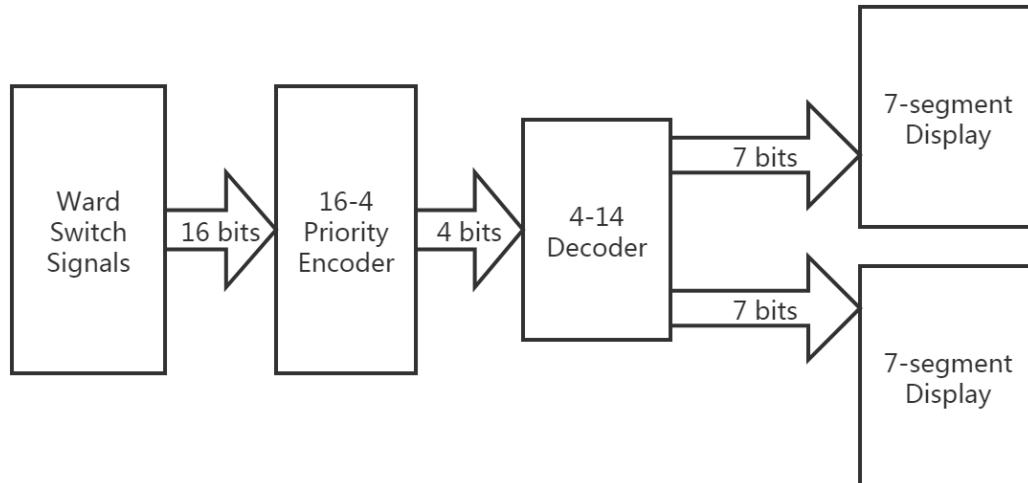

Code

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity encoder_16_4 is
5  port (encoder_in: in std_logic_vector(15 downto 0);
6       encoder_out: out std_logic_vector(3 downto 0));
7  end encoder_16_4;
8
9  architecture design_encoder_16_4 of encoder_16_4 is
10 begin
11
12     encoder_out <= "0000" when encoder_in(15) = '1' else
13                    "1111" when encoder_in(14) = '1' else
14                    "1110" when encoder_in(13) = '1' else
15                    "1101" when encoder_in(12) = '1' else
16                    "1100" when encoder_in(11) = '1' else
17                    "1011" when encoder_in(10) = '1' else
18                    "1010" when encoder_in(9) = '1' else
19                    "1001" when encoder_in(8) = '1' else
20                    "1000" when encoder_in(7) = '1' else
21                    "0111" when encoder_in(6) = '1' else
22                    "0110" when encoder_in(5) = '1' else
23                    "0101" when encoder_in(4) = '1' else
24                    "0100" when encoder_in(3) = '1' else
25                    "0011" when encoder_in(2) = '1' else
26                    "0010" when encoder_in(1) = '1' else
27                    "0001" when encoder_in(0) = '1' else
28                    "0000";
29
30 end design_encoder_16_4;

```

```

32 library ieee;
33 use ieee.std_logic_1164.all;
34
35 entity decoder_4_14 is
36 port (decoder_in: in std_logic_vector(3 downto 0);
37       decoder_out: out std_logic_vector(13 downto 0));
38 end decoder_4_14;
39
40 architecture design_decoder_4_14 of decoder_4_14 is
41 begin
42   with decoder_in select
43     decoder_out <= "1111101111110" when "0000",
44                   "1111100110000" when "0001",
45                   "1111101101101" when "0010",
46                   "1111101111001" when "0011",
47                   "1111100110011" when "0100",
48                   "1111101011011" when "0101",
49                   "1111101011111" when "0110",
50                   "1111101110000" when "0111",
51                   "1111101111111" when "1000",
52                   "1111101111011" when "1001",
53
54                   "0110000111110" when "1010",
55                   "01100000110000" when "1011",
56                   "01100001101101" when "1100",
57                   "01100001111001" when "1101",
58                   "01100000110011" when "1110",
59                   "01100001011011" when "1111",
60
61                   "00000000000000" when others;
62 end design_decoder_4_14;


```

```

64 library ieee;
65 use ieee.std_logic_1164.all;
66
67 entity ward_switch_15 is
68 port( input: in std_logic_vector(15 downto 0);
69       output: out std_logic_vector(13 downto 0);
70       signal_4: out std_logic_vector(3 downto 0));
71 end ward_switch_15;
72
73 architecture design_ward of ward_switch_15 is
74
75 component encoder_16_4 is
76 port (encoder_in: in std_logic_vector(15 downto 0);
77       encoder_out: out std_logic_vector(3 downto 0));
78 end component;
79
80 component decoder_4_14 is
81 port (decoder_in: in std_logic_vector(3 downto 0);
82       decoder_out: out std_logic_vector(13 downto 0));
83 end component;
84
85 signal encoder_4 : std_logic_vector(3 downto 0);
86
87 begin
88   encoder: encoder_16_4 port map (input, encoder_4);
89   decoder: decoder_4_14 port map (encoder_4, output);
90
91   signal_4 <= encoder_4;
92
93 end design_ward;

```

Test

 

As shown, “input” is an 16-bit signal that shows which wards have alerted. The most left bit represents ward number 1.

“signal” is a 4-bit signal produced by 16-4 encoder. It shows the priority number of wards.

“output” is a 14-bit signal which can be separate to two 7-bits parts and be sent to two 7-segment displays to show the corresponding number.

