 


# 1. Majority circuit

a) Truce Table:

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1


K-map:



Boolean equation:

$$F = AC + AB + BC$$

Logic Circuit:

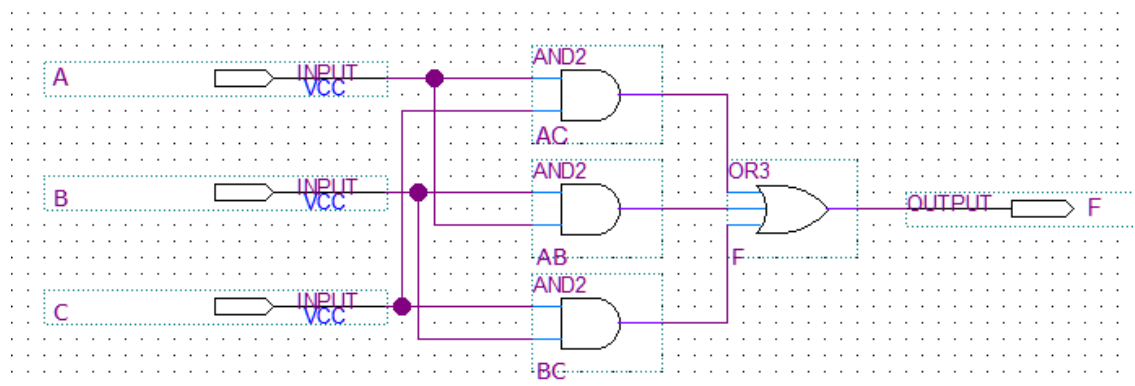

b) VHDL code:

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity and_2 is
5  port ( a1, a2 : in std_logic;
6         F_and_2 : out std_logic );
7  end and_2;
8
9  architecture design_and_2 of and_2 is
10 begin
11     F_and_2 <= a1 and a2;
12 end design_and_2;
13
14 library ieee;
15 use ieee.std_logic_1164.all;
16
17 entity or_3 is
18 port ( o1, o2, o3 : in std_logic;
19        F_or_3 : out std_logic );
20 end or_3;
21
22 architecture design_or_3 of or_3 is
23 begin
24     F_or_3 <= o1 or o2 or o3;
25 end design_or_3;
26


```

```

26
27 library ieee;
28 use ieee.std_logic_1164.all;
29
30 entity A1_Task1 is
31   port( A, B, C : in std_logic;
32         F       : out std_logic );
33 end A1_Task1;
34
35
36 architecture design of A1_Task1 is
37
38   component and_2
39   port ( a1, a2 : in std_logic;
40         F_and_2 : out std_logic );
41 end component;
42
43   component or_3
44   port ( o1, o2, o3 : in std_logic;
45         F_or_3     : out std_logic );
46 end component;
47
48   signal out1, out2, out3 : std_logic;
49
50 begin
51   A1: and_2 port map (A, C, out1);
52   A2: and_2 port map (A, B, out2);
53   A3: and_2 port map (B, C, out3);
54   O1: or_3  port map (out1, out2, out3, F);
55 end design;

```

Test Bench:

 

## 2. Subtractor Circuit

a) Equation of full adders:

$$\text{Sum} = x \oplus y \oplus \text{Cin}$$

$$\text{Cout} = x*y + \text{Cin}*x + \text{Cin}*y$$

For subtractor, use full adders and let:

$$y = y'$$

$$\text{Cin} = 1$$

VHDL code:

```

1 library ieee;
2 use ieee.std_logic_1164.all;
3
4 entity adder is
5   port (X, Y, Cin : in std_logic;
6         Cout, Sum : out std_logic);
7 end adder;
8
9 architecture eq of adder is
10 begin
11   Sum <= X xor Y xor Cin;
12   Cout <= (X and Y) or (X and Cin) or (Y and Cin);
13 end eq;
14
15


```

```

16 library ieee;
17 use ieee.std_logic_1164.all;
18
19 entity Subtractor_1 is
20     port (X, Y, Cin : in std_logic;
21           Cout, Sum : out std_logic);
22 end Subtractor_1;
23
24 architecture sub of Subtractor_1 is
25     component adder
26     port (X, Y, Cin : in std_logic;
27           Cout, Sum : out std_logic);
28     end component;
29 begin
30     sub1 : adder port map (X, not Y, '1', Cout, Sum);
31 end sub;
32

```

b) Test bench:

 

c) 4-bit subtractor:


VHDL code:

```

33 library ieee;
34 use ieee.std_logic_1164.all;
35
36 entity Subtractor is
37     port (X, Y : in std_logic_vector (3 downto 0);
38           Cin : in std_logic;
39           Cout : out std_logic;
40           Sum : out std_logic_vector (3 downto 0));
41 end Subtractor;
42
43 architecture sub4 of Subtractor is
44     component adder
45     port (X, Y, Cin : in std_logic;
46           Cout, Sum : out std_logic);
47     end component;
48
49     signal c : std_logic_vector (3 downto 1);
50 begin
51     sub1 : adder port map (X(0), not Y(0), '1', c(1), Sum(0));
52     sub2 : adder port map (X(1), not Y(1), c(1), c(2), Sum(1));
53     sub3 : adder port map (X(2), not Y(2), c(2), c(3), Sum(2));
54     sub4 : adder port map (X(3), not Y(3), c(3), Cout, Sum(3));
55 end sub4;


```

d) test bench:

 

3. 16x1 mux

a) Block diagram

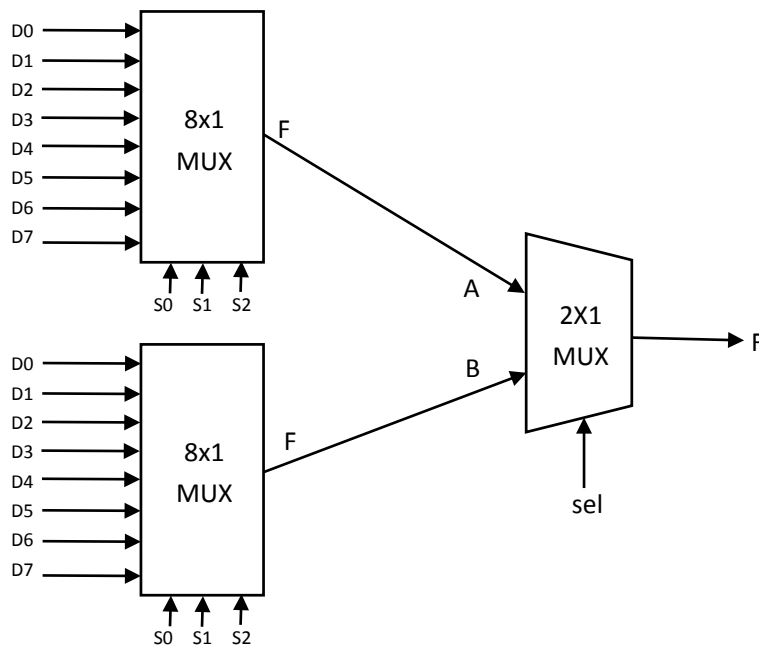

b) VHDL code:

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity and_2 is
5  port ( a1, a2 : in std_logic;
6         F_and_2 : out std_logic );
7  end and_2;
8
9  architecture design_and_2 of and_2 is
10 begin
11     F_and_2 <= a1 and a2;
12 end design_and_2;
13
14 library ieee;
15 use ieee.std_logic_1164.all;
16
17 entity and_4 is
18 port ( a1, a2, a3, a4 : in std_logic;
19        F_and_4       : out std_logic );
20 end and_4;
21
22 architecture design_and_4 of and_4 is
23 begin
24     F_and_4 <= a1 and a2 and a3 and a4;
25 end design_and_4;

```

```

26  L
27  library ieee;
28  use ieee.std_logic_1164.all;
29
30  entity or_2 is
31  port ( o1, o2      : in std_logic;
32        F_or_2      : out std_logic );
33  end or_2;
34
35  architecture design_or_2 of or_2 is
36  begin
37      F_or_2 <= o1 or o2;
38  end design_or_2;
39
40  library ieee;
41  use ieee.std_logic_1164.all;
42
43  entity or_8 is
44  port ( o1, o2, o3, o4, o5, o6, o7, o8 : in std_logic;
45        F_or_8                        : out std_logic );
46  end or_8;
47
48  architecture design_or_8 of or_8 is
49  begin
50      F_or_8 <= o1 or o2 or o3 or o4 or o5 or o6 or o7 or o8;
51  end design_or_8;
52
53  library ieee;
54  use ieee.std_logic_1164.all;
55
56  entity inv is
57  port (i1      : in std_logic;
58        F_inv   : out std_logic );
59  end inv;
60
61  architecture design_inv of inv is
62  begin
63      F_inv <= not i1;
64  end design_inv;
65
66  library ieee;
67  use ieee.std_logic_1164.all;
68
69  entity mux8 is
70  port (s0, s1, s2
71        d0, d1, d2, d3, d4, d5, d6, d7 : in std_logic;
72        F_mux8                        : out std_logic );
73  end mux8;
74
75  architecture design_mux8 of mux8 is
76  |
77  component and_4 is
78  port ( a1, a2, a3, a4 : in std_logic;
79        F_and_4       : out std_logic );
80  end component;
81  |
82  component or_8 is
83  port ( o1, o2, o3, o4, o5, o6, o7, o8 : in std_logic;
84        F_or_8                        : out std_logic );
85  end component;
86  |
87  component inv is
88  port (i1      : in std_logic;
89        F_inv   : out std_logic );
90  end component;
91  |
92  signal s0_bar, s1_bar, s2_bar, out1, out2, out3, out4, out5, out6, out7, out8 : std_logic;
93
94  begin
95      inv0: inv port map (s0, s0_bar);
96      inv1: inv port map (s1, s1_bar);
97      inv2: inv port map (s2, s2_bar);
98

```

```

99  A1:  and_4 port map (d0, s0_bar, s1_bar, s2_bar, out1);
100 A2:  and_4 port map (d1, s0_bar, s1_bar, s2, out2);
101 A3:  and_4 port map (d2, s0_bar, s1, s2_bar, out3);
102 A4:  and_4 port map (d3, s0_bar, s1, s2, out4);
103 A5:  and_4 port map (d4, s0, s1_bar, s2_bar, out5);
104 A6:  and_4 port map (d5, s0, s1_bar, s2, out6);
105 A7:  and_4 port map (d6, s0, s1, s2_bar, out7);
106 A8:  and_4 port map (d7, s0, s1, s2, out8);
107
108 O1:  or_8 port map (out1, out2, out3, out4, out5, out6, out7, out8, F_mux8);
109
110 end design_mux8;
111
112 library ieee;
113 use ieee.std_logic_1164.all;
114
115 entity mux2 is
116 port(sel      : in  std_logic;
117       a, b     : in  std_logic;
118       F_mux2: out  std_logic );
119 end mux2;
120
121 architecture design_mux2 of mux2 is
122
123 component and_2 is
124 port ( a1, a2 : in  std_logic;
125       F_and_2 : out std_logic );
126 end component;
127
128 component or_2 is
129 port ( o1, o2 : in  std_logic;
130       F_or_2  : out std_logic );
131 end component;
132
133 component inv is
134 port (i1      : in  std_logic;
135       F_inv   : out  std_logic );
136 end component;
137
138 signal sel_bar, out1, out2 : std_logic;
139
140 begin
141
142 inv0: inv port map (sel, sel_bar);
143
144 A1:  and_2 port map (a, sel_bar, out1);
145 A2:  and_2 port map (b, sel, out2);
146
147 O1:  or_2 port map (out1, out2, F_mux2);
148
149 end design_mux2;
150
151 library ieee;
152 use ieee.std_logic_1164.all;
153
154 entity mux16 is
155 port (s0, s1, s2, s3      : in  std_logic;
156       d0, d1, d2, d3, d4, d5, d6, d7 : in  std_logic;
157       d8, d9, d10, d11, d12, d13, d14, d15 : in  std_logic;
158       F_mux16 : out  std_logic );
159 end mux16;
160
161 architecture design_mux16 of mux16 is
162
163 component mux8 is
164 port (s0, s1, s2      : in  std_logic;
165       d0, d1, d2, d3, d4, d5, d6, d7 : in  std_logic;
166       F_mux8 : out  std_logic );
167 end component;
168
169 component mux2 is
170 port(sel      : in  std_logic;
171       a, b     : in  std_logic;
172       F_mux2: out  std_logic );
173 end component;
174

```

```

175 signal F1, F2 : std_logic;
176
177 begin
178 mux8_1 : mux8 port map (s1, s2, s3, d0, d1, d2, d3, d4, d5, d6, d7, F1);
179 mux8_2 : mux8 port map (s1, s2, s3, d8, d9, d10, d11, d12, d13, d14, d15, F2);
180
181 mux2_1 : mux2 port map (s0, F1, F2, F_mux16);
182
183 end design_mux16;
184
185
186

```

c) Test bench

