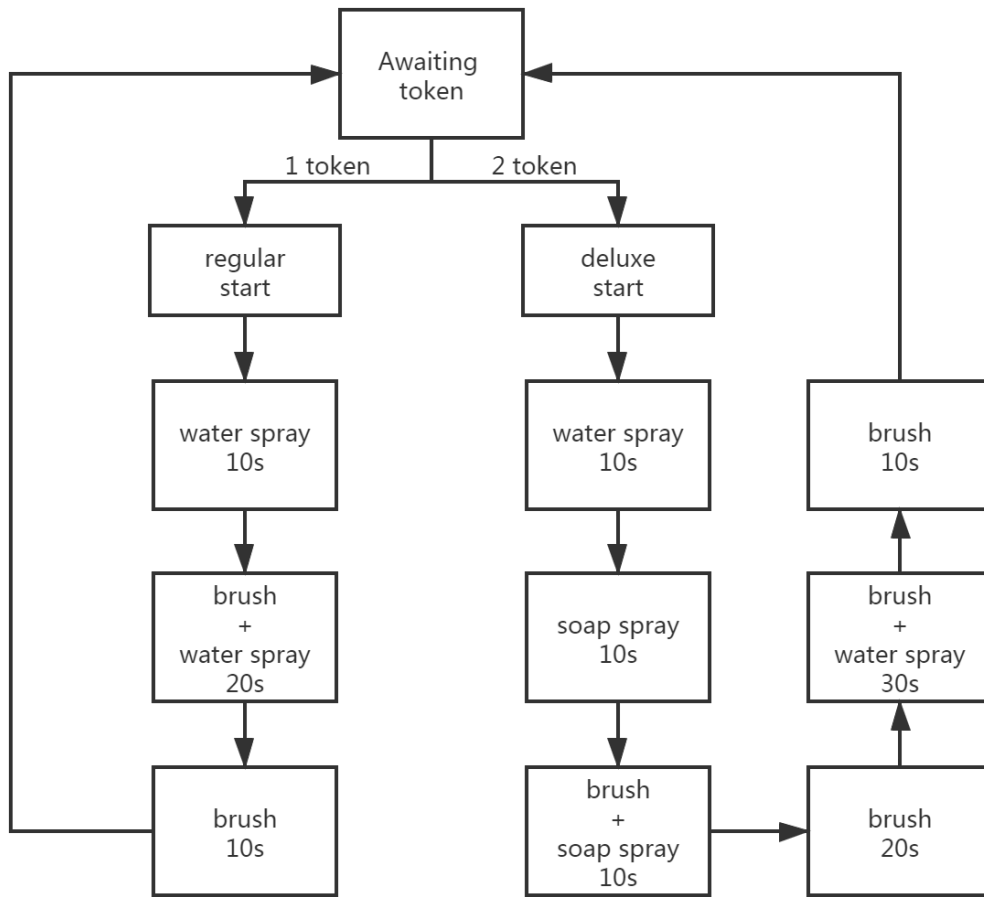


1.

Block diagram:



2.

Regular system

State diagram:

State:

S0: initial state

S1: 10s water spray

S2: 20s water spray + brush


S4: 10s brush

Output:

Water spray: 10

Brush: 01

Water spray + brush: 11

 

Code:

5bit counter:

```
counter5bit.vhd      regular.vhd
1  library ieee ;
2  use ieee . std_logic_1164 . all ;
3  use ieee . numeric_std . all ;
4  ENTITY counter5bit IS
5  PORT ( clk , rst : in std_logic ;
6        q: out std_logic_vector (4 downto 0));
7  END counter5bit;
8
9  ARCHITECTURE rtl OF counter5bit IS
10 signal cnt : unsigned (4 downto 0) := "00001";
11 BEGIN
12 process (clk)
13 begin
14     if (clk'event and clk = '1') then
15         if (rst='1') then
16             cnt <= "00001";
17         else
18             cnt <= cnt + "1";
19         end if ;
20     end if ;
21 end process ;
22 q <= std_logic_vector ( cnt );
23 END rtl ;
```

Regular wash:


```
1  library ieee; use ieee.std_logic_1164.all;
2
3  ENTITY regular IS
4  PORT( clk, token_1 : IN STD_LOGIC;|
5        water, brush : OUT STD_LOGIC);
6  END regular;
7
8  ARCHITECTURE design OF regular IS
9  component counter5bit is
10 port ( clk , rst : in std_logic ;
11       q: out std_logic_vector (4 downto 0) );
12 end component;
13
14 signal start_timer, time_10sec, time_20sec: std_logic;
15 signal q_out : std_logic_vector (4 downto 0);
16
17 -- Declare a state type
18 type state_type is (Initial, W10s, WB20s, B10s);
19
20 -- Declare current and next state variables .
21 signal current_state , next_state : state_type := Initial;
22
23 BEGIN
24
25 t0 : counter5bit port map ( clk , start_timer , q_out );
26
27 time_10sec <= q_out (3) and q_out (1);
28 time_20sec <= q_out (4) and q_out (2);
29
30 process ( clk )
31 begin
32     if (clk'event and clk='1') then
33         current_state <= next_state ;
34     end if ;
35 end process ;
36 -- Process to determine next state
37
38 process ( current_state, time_10sec, time_20sec)
39 begin
40     case current_state is
41     when Initial =>
42         if (token_1 = '1') then
43             next_state <= W10s ;
44         else
45             next_state <= current_state;
46         end if ;
```

```

47
48   when W10s =>
49       if (time_10sec = '1') then
50           next_state <= WB20s ;
51       else
52           next_state <= current_state;
53       end if ;
54
55   when WB20s =>
56       if (time_20sec = '1') then
57           next_state <= B10s ;
58       else
59           next_state <= current_state;
60       end if ;
61
62   when B10s =>
63       if (time_10sec = '1') then
64           next_state <= Initial ;
65       else
66           next_state <= current_state;
67       end if ;
68
69 end case ;
70 end process ;
71
72 -- Conditional assignments for outputs:
73 water <= '1' when ((current_state = W10s) or (current_state = WB20s)) else '0';
74 brush <= '1' when ((current_state = B10s) or (current_state = WB20s)) else '0';
75
76 start_timer <= '1' when (current_state /= next_state) else '0';
77
78 END design ;
79

```

Test: 2 times of regular wash

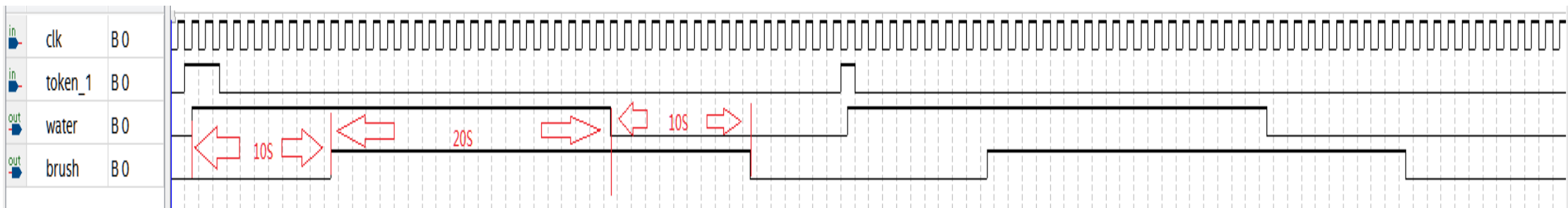

## Deluxe + Regular

State diagram:

State:

S0: initial state

S11: 10s water spray

S12: 20s water spray + brush

S13: 10s brush

S21: 10s water spray

S22: 10s soap spray

S23: 10s soap spray + brush

S24: 20s brush

S25: 30s water spray + brush

S26: 10s brush

Output:


Water spray: 010

Brush: 001

Soap: 100

Water spray + brush: 011

Soap spray + brush: 101

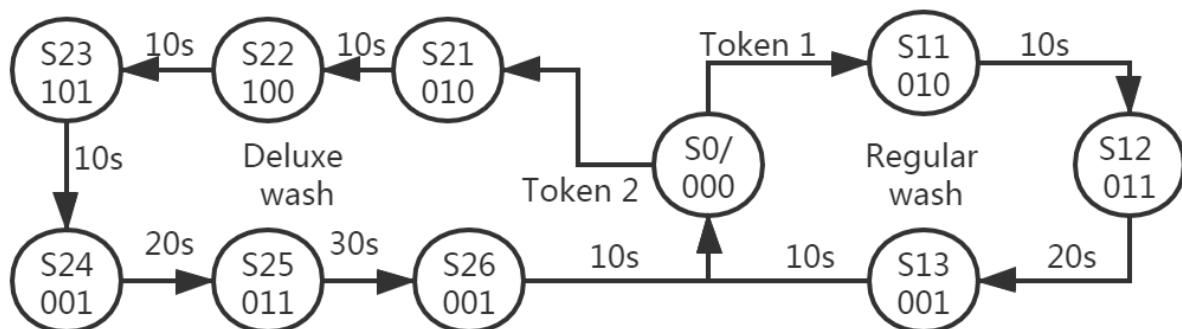

Code:

```

1  library ieee; use ieee.std_logic_1164.all;
2
3  ENTITY Deluxe_Regular IS
4  PORT( clk, token_1, token_2 : IN STD_LOGIC;
5        soap, water, brush : OUT STD_LOGIC);
6  END Deluxe_Regular;
7
8  ARCHITECTURE design OF Deluxe_Regular IS
9  component counter5bit is
10 port ( clk , rst : in std_logic ;
11        q: out std_logic_vector (4 downto 0) );
12 end component;
13
14 signal start_timer, time_10sec, time_20sec, time_30sec: std_logic;
15 signal q_out : std_logic_vector (4 downto 0);
16
17 -- Declare a state type
18 type state_type is (Initial, s11, s12, s13,
19                    s21, s22, s23, s24, s25, s26);
20

```

```

20 |
21 | -- Declare current and next state variables .
22 | signal current_state , next_state : state_type := Initial;
23 |
24 | BEGIN
25 |
26 | t0 : counter5bit port map ( clk , start_timer , q_out );
27 |
28 | time_10sec <= q_out (3) and q_out (1);
29 | time_20sec <= q_out (4) and q_out (2);
30 | time_30sec <= q_out (4) and q_out (3) and q_out (2) and q_out (1);
31 |
32 | process ( clk )
33 | begin
34 |   if (clk'event and clk='1') then
35 |     current_state <= next_state ;
36 |   end if ;
37 | end process ;
38 | -- Process to determine next state
39 |
40 | process ( current_state, time_10sec, time_20sec, time_30sec)
41 | begin
42 |   case current_state is
43 |   when Initial =>
44 |     if (token_2 = '1') then
45 |       next_state <= s21 ;
46 |     elsif (token_1 = '1') then
47 |       next_state <= s11 ;
48 |     else
49 |       next_state <= current_state;
50 |     end if ;
51 |
52 |   when s11 =>
53 |     if (time_10sec = '1') then
54 |       next_state <= s12 ;
55 |     else
56 |       next_state <= current_state;
57 |     end if ;

```

```

58 |
59 |   when s12 =>
60 |     if (time_20sec = '1') then
61 |       next_state <= s13 ;
62 |     else
63 |       next_state <= current_state;
64 |     end if ;
65 |
66 |   when s13 =>
67 |     if (time_10sec = '1') then
68 |       next_state <= Initial ;
69 |     else
70 |       next_state <= current_state;
71 |     end if ;
72 |
73 |   when s21 =>
74 |     if (time_10sec = '1') then
75 |       next_state <= s22 ;
76 |     else
77 |       next_state <= current_state;
78 |     end if ;
79 |
80 |   when s22 =>
81 |     if (time_10sec = '1') then
82 |       next_state <= s23 ;
83 |     else
84 |       next_state <= current_state;
85 |     end if ;
86 |
87 |   when s23 =>
88 |     if (time_10sec = '1') then
89 |       next_state <= s24 ;
90 |     else
91 |       next_state <= current_state;
92 |     end if ;

```

```

93
94     when s24 =>
95         if (time_20sec = '1') then
96             next_state <= s25 ;
97         else
98             next_state <= current_state;
99         end if ;
100
101     when s25 =>
102         if (time_30sec = '1') then
103             next_state <= s26 ;
104         else
105             next_state <= current_state;
106         end if ;
107
108     when s26 =>
109         if (time_10sec = '1') then
110             next_state <= Initial ;
111         else
112             next_state <= current_state;
113         end if ;
114
115 end case ;
116 end process ;
117
118 -- Conditional assignments for outputs:
119 soap <= '1' when ((current_state = s22) or (current_state = s23)) else '0';
120
121 water <= '1' when ((current_state = s11) or (current_state = s12)
122                  or (current_state = s21) or (current_state = s25)) else '0';
123
124 brush <= '1' when ((current_state = s12) or (current_state = s13)
125                  or (current_state = s23) or (current_state = s24)
126                  or (current_state = s25) or (current_state = s26)) else '0';
127
128 start_timer <= '1' when (current_state /= next_state) else '0';
129
130 END design ;

```

Test: 1 time of regular wash, then 1 time of deluxe wash:

